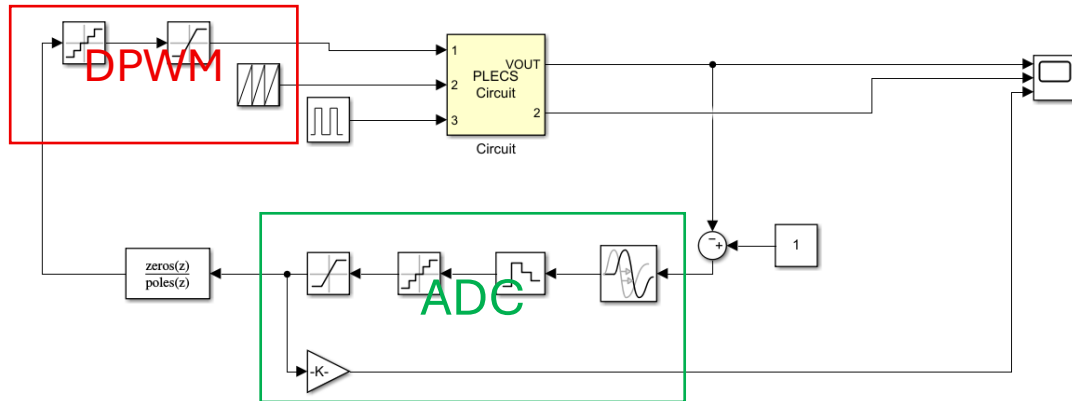


Digitally Controlled Voltage Mode Buck Converter

Report

A. Functional Blocks and Key Design Considerations



i. Analog-to-Digital Converter (ADC)


- Pipeline latency:** total delay $t = t_{\text{conv}} + t_{\text{cal}} + t_g$. With $t_{\text{conv}} = 420 \text{ ns}$, $t_{\text{cal}} = 65 \text{ ns}$, $t_g = 10 \text{ ns} \Rightarrow$ **loop delay $\approx 495 \text{ ns}$.**
- Sample-and-hold (ZOH):** sampling period $T_s = 1/f_{\text{sw}} = 2 \mu\text{s}$
- Resolution:** 7-bit $\Rightarrow \text{LSB } \Delta V_q = V_{\text{FS}}/2^7 = 15.625 \text{ mV}$
- Saturation:** output clamped to $\pm 4 \text{ LSB}$, i.e. $-62.5 \text{ mV} \dots +62.5 \text{ mV}$.
- Designed for 1 MHz switching.

ii. Digital PWM (DPWM)

- Resolution: **9 bits.**
- Duty-cycle quantization step derived accordingly.
- Higher resolution chosen to minimize limit-cycle oscillation (LCO).

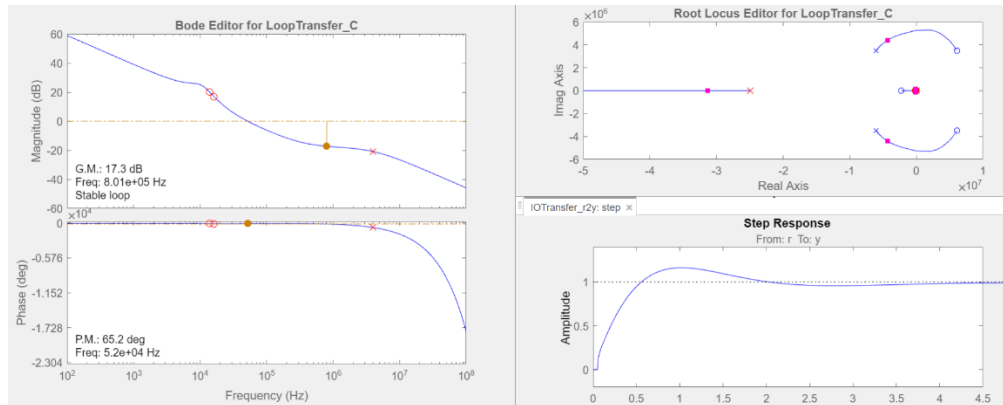B. Digital Compensator Design

- Place desired poles/zeros in the plant transfer function while accounting for the 495 ns loop delay to meet bandwidth and stability specs.




- ii. Export analogue compensator into MATLAB, perform s-to-z transformation with prewarp to obtain the discrete transfer function in the form required by the digital controller.

C. Closed-Loop Simulation (Power Stage + ADC + DPWM + Compensator)


i. Time-Domain Results:

 - a. Overall waveform shows inductor current varying smoothly between 0.5 A and 1 A.




- b. Transient response: Light-to-heavy load step and heavy-to-light step behave as predicted.

 1. Transfer from Light load to heavy load




 2. Transfer from heavy load to Light load



ii. Steady state:

 
- a. Verified at 1 A and 0.5 A; voltage and current ripple within spec.



D. Limit-Cycle Oscillation (LCO) Simulation


- i. A1: Reduce DPWM resolution from 9 bits to **5 bits** → quantisation too coarse.

- a. Waveform: Pronounced LCO appears.

 

- ii. A2: Double compensator gain so output is no longer properly limited.

 - a. Waveform: Control loop becomes unstable, exhibiting oscillatory behavior.



E. Submission Package

- i. Report.pdf
- ii. DBE.m
- iii. Model.mdl