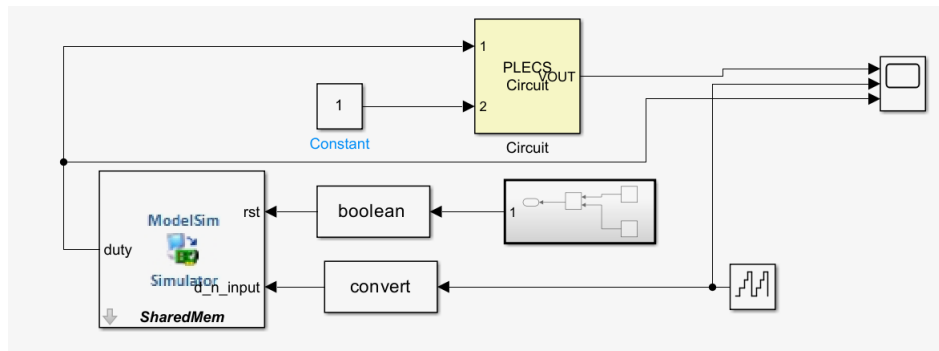


Realization of DPWM Report


1. System

- A. This system also uses Simulink and ModelSim for co-simulation. The figure below shows the block diagram of this system, where the comparator inside PLECS is replaced with the output result of digital circuits. The open-loop behavior of the 9-bit counter DPWM is simulated. By using Verilog to model the digital circuit behavior, the impacts and differences of three DPWM methods—**Counter DPWM, Hybrid DPWM, and Dither DPWM**—on the system are observed. The counter free-running is set to 9 bits, and the sample time is set to $1e-3$ as provided in the handout.



2. Counter DPWM

 
- A. Implemented through counterbase.v. In this design, both d_n_input and count are set to 9 bits, and the counter resets to zero when overflow occurs. During co-simulation, since DPWM is 9 bits, the duty sample frequency is set to $2^9 * 500k$, and the clock (clk) is also set to $2^9 * 500k$.



- B. As seen in the waveform diagram above, the output voltage v_o increases with the rise of the digital circuit voltage, oscillating according to the duty. The simulation results match the expected behavior.

3. Hybrid DPWM

 
- A. The original 9-bit counter DPWM is split into a 6-bit counter plus a 3-bit delay line. Since the counter is reduced to 6 bits, the clock frequency is adjusted to $2^6 * 500k$.



- B. During simulation, a duty period of $4e-9$ caused the circuit to miss voltage changes, so it was modified to $2e-9$. As seen in the waveform diagram above, the output voltage V_o increases with the digital circuit voltage and oscillates with the duty. The simulation results are as expected.

4. Dither DPWM

 - A. In this design, the table-based output generates ditherin. Overflow handling must be addressed. Thus, the condition inside the if statement resets to zero when $\text{count} = 3'b111$.




- B. The co-simulation setup is the same as earlier cases. Observation of the waveform diagram also confirms that the simulation results meet expectations.

5. Dither DPWM with Dead-Time

 - A. After adding dead-time, the counter module in the top file is replaced with a dead-time module. duty_high and duty_low are used instead of the original

duty function, with their sample time set to $2e-9$.



- B. Because two MOSFETs are operated separately, the NOT logic gate in PLECS can be removed. The rest of the configuration remains the same.
 - C. From the waveform results, it is observed that `duty_high` and `duty_low` switch between each other, ensuring only one MOSFET is on at a time. The final output `vo` matches the expected performance.
6. **Submission Materials**
- A. Lab report document (Lab4_StudentID.docx)
 - B. Verilog file (.v)